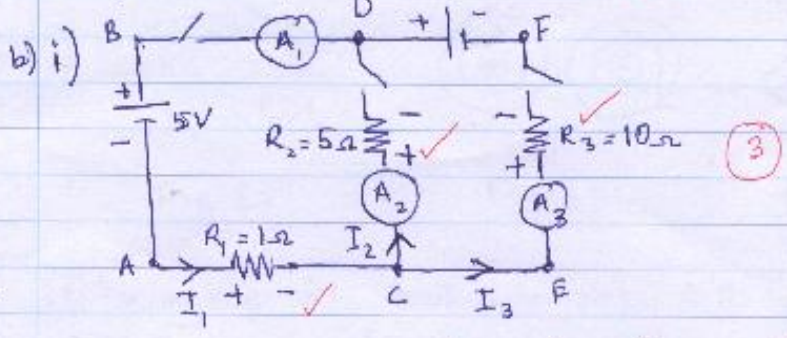


- (i) 3
- (ii) 4

(iii) $5+3+2+6+4+3 = 23$

Question 1



(ii) At D; $\sum I_{in} = \sum I_{out}$. $I_2 + I_3 = I_1$ - [1] - (4)

(iii) Loop BDCAB: $\sum V_{drop} = \sum V_{rise}$
 $0 = 5I_2 + I_1 + 5V$ - [2] - (5)

Loop DFECDF: $\sum V_{drop} = \sum V_{rise}$
 $10V + 5I_2 = 10I_3$ - [3] - (3)

Substitute [1] into [2]: $-5V = 5I_2 + I_2 + I_3$ - (2)
 $-5V = 6I_2 + I_3$ - [4]
 $10V = -5I_2 + 10I_3$ - [3]

Remove I_3 . So multiply [4] by 10 then subtract [3]
 $-50V = 60I_2 + 10I_3$ - [5]
 $10V = -5I_2 + 10I_3$ - [3] (6)

So, [5] - [3]: $-60V = 65I_2$; So, $I_2 = -\frac{60}{65} = -\frac{12}{13} A$
 Since I_2 is -ve, it indicates that the direction of I_2 is opposite the direction we chose.

Substitute I_2 into [4]: $-5V = 6\left(\frac{12}{13}\right) + I_3$. So, $I_3 = -\frac{65+72}{13} A$ (4)

$I_3 = -\frac{7}{13} A$. Again, I_3 is opposite the direction we initially chose. (3)
 From [1], $I_1 = I_2 + I_3 = -\frac{12}{13} - \frac{7}{13} = -\frac{19}{13} A = -1.46 A$. I_1 in opposite direction.

Test 2 - Set 1

Question 2

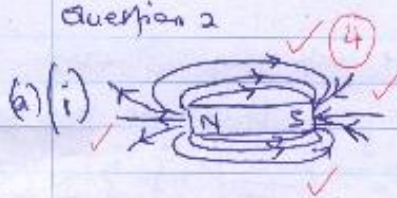


Fig 3a

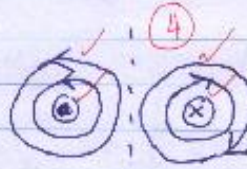


Fig 3b



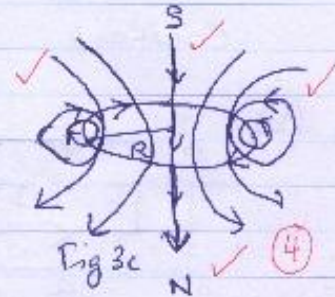


Fig 3c

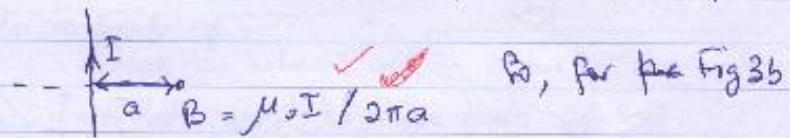(ii) For a long wire, B at a horizontal distance a from the wire is



$$B = \frac{\mu_0 I}{2\pi a}$$

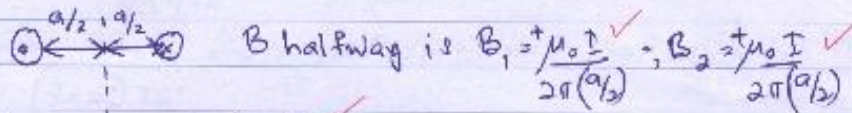

B halfway is $B_1 = \frac{\mu_0 I}{2\pi(a/2)}$; $B_2 = \frac{\mu_0 I}{2\pi(a/2)}$

Both B 's pointing up determined using 2nd RHR.

$$B = B_1 + B_2 = \frac{\mu_0 I}{2\pi a}$$

(6)


(iii) The wire loop behaves like a bar magnet and based on the field lines drawn, then South pole is above the wire. At the center of the coil $B = \frac{\mu_0 I}{2R}$

(a) - [12] + (b) - [26] = 38


Q1 - 38
 Q2 - 38
 74

PHY 407 - Apr 2nd 2009 Question Number
 Test 2 - Set 1 (a) - 8


Question 1

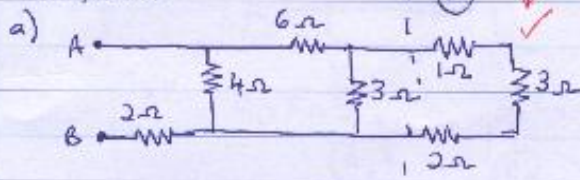

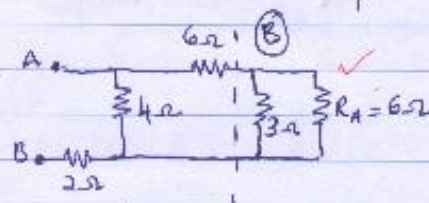
either diagram or
 For section A, R in series.
 $R_0, R_A = 1\Omega + 3\Omega + 2\Omega = 6\Omega$



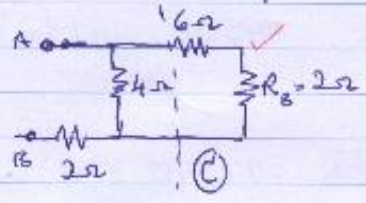
R_B in parallel. So,
 $\frac{1}{R_B} = \frac{1}{3\Omega} + \frac{1}{6\Omega} = \frac{2+1}{6\Omega} = \frac{1}{2\Omega}$. So $R_B = 2\Omega$



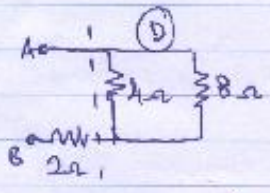For section C, R in series.
 So, $R_C = 6\Omega + 2\Omega = 8\Omega$



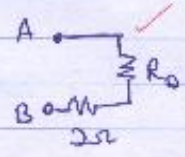For section D, R in parallel
 So, $\frac{1}{R_D} = \frac{1}{4\Omega} + \frac{1}{8\Omega} = \frac{3}{8\Omega}$. So, $R_D = \frac{8}{3}\Omega$



Hence between points A & B, we now have
 2 resistors in series. So, $R_T = 2\Omega + \frac{8}{3}\Omega = \frac{14}{3}\Omega$
 So, $R_T = \frac{14}{3}\Omega = 4.67\Omega$

~~8~~ 10

Q1 (a) - 8 + (b) - 30 = 48

Test Question 2 - Set 1

Question 2

(or stating B out of page)

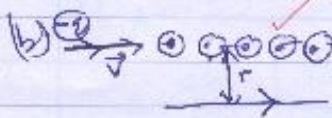




Fig 5(i)

(6)

$$B = \frac{\mu_0 I}{2\pi r}$$

Using RHR #1, F downwards if q is +ve. Since q is -ve, then F is upwards.

$$F = qvB = \frac{qv\mu_0 I}{2\pi r}$$

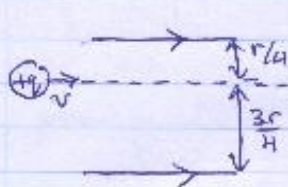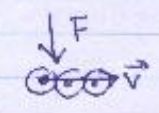

Along the line of motion B due to top wire is

$$B = \frac{\mu_0 I}{2\pi(r/4)} \text{ into the page, } (\otimes)$$

B due to bottom wire is, $B = \frac{\mu_0 I}{2\pi(3r/4)}$, out of page.

Let B into page is +ve

$$\text{then } B = +\frac{\mu_0 I}{2\pi(r/4)} + \left(-\frac{\mu_0 I}{2\pi(3r/4)}\right) = \frac{\mu_0 I}{2\pi(r/4)} \left[1 - \frac{4}{3}\right] = -\frac{\mu_0 I}{2\pi r} \left(\frac{1}{3}\right)$$


out of page.

out of page


OR

Note: if choose B out of page as +ve then the answer is +ve which means out of page.

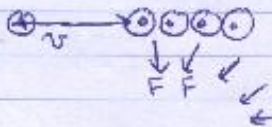then F on the charged particle is $F = qvB = qv \left(\frac{2\mu_0 I}{3\pi r}\right)$ down




(7)

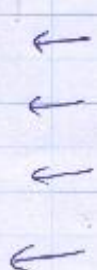

Test 2 - Set 1

Question 2

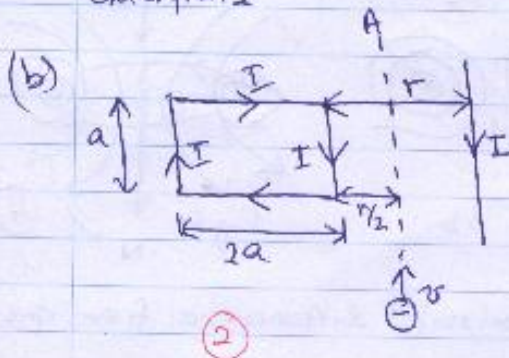

choose info page as +ve.
So, along A, B due to long wire
is $B_w = +\frac{\mu_0 I}{2\pi(\frac{r}{2})}$ info page (x)

For the loop, consider only wires that are parallel or antiparallel to direction of motion for charge.

For the right wire of loop; $B = \frac{\mu_0 I}{2\pi(r/2)}$ out of page. (4)

For the left wire of the loop, $B = \frac{\mu_0 I}{2\pi(2a+r/2)}$ info page.

Hence, $B = \frac{\mu_0 I}{2\pi(r/2)} + \frac{\mu_0 I}{2\pi(2a+r/2)} + \left(-\frac{\mu_0 I}{2\pi(r/2)}\right) = \frac{\mu_0 I}{2\pi(2a+r/2)}$ info page.

Then the force F on the charge is $F = qvB$ to the left if q is +ve.

Since q is -ve, then $F = qv \frac{\mu_0 I}{2\pi(2a+r/2)}$ to the left. (7)

(b) - 6 + 7 + 73 = 26